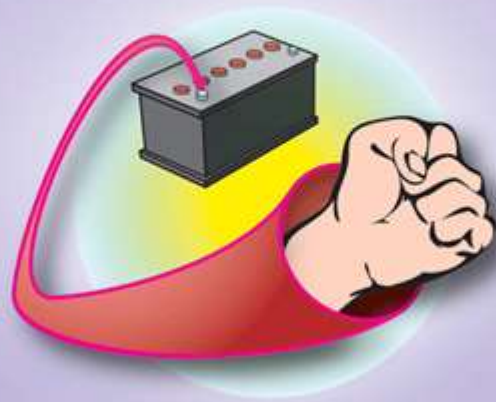


BASIC ELECTRICITY for PVs

Part One: Volts, Amps, Watts
Series and Parallel Wiring

Volts, Amps, Watts

VOLT
(FORCE)



**MEASURES ELECTRICAL
PRESSURE**


VOLTS

- Difference causes “force”
- Electromotive Force
- Water Analogy: “Pressure”

High Volts or Low Volts?



AMPERE (CURRENT)

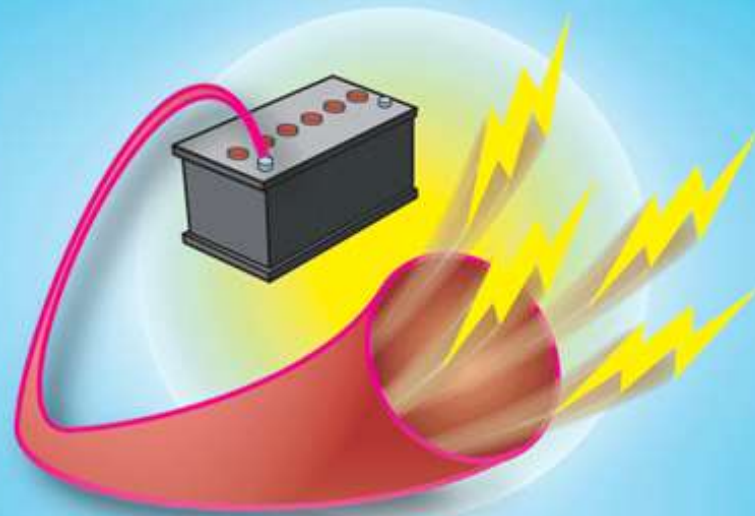


**MEASURES THE NUMBER
OF MOVING ELECTRONS
(OR ELECTRIC CHARGES)**

Courtesy Clay Atcheson

AMPS


- Current, Flow of Electrical Charges
- Only measurable when circuit is closed (on)
- Water Analogy: GPM, volume

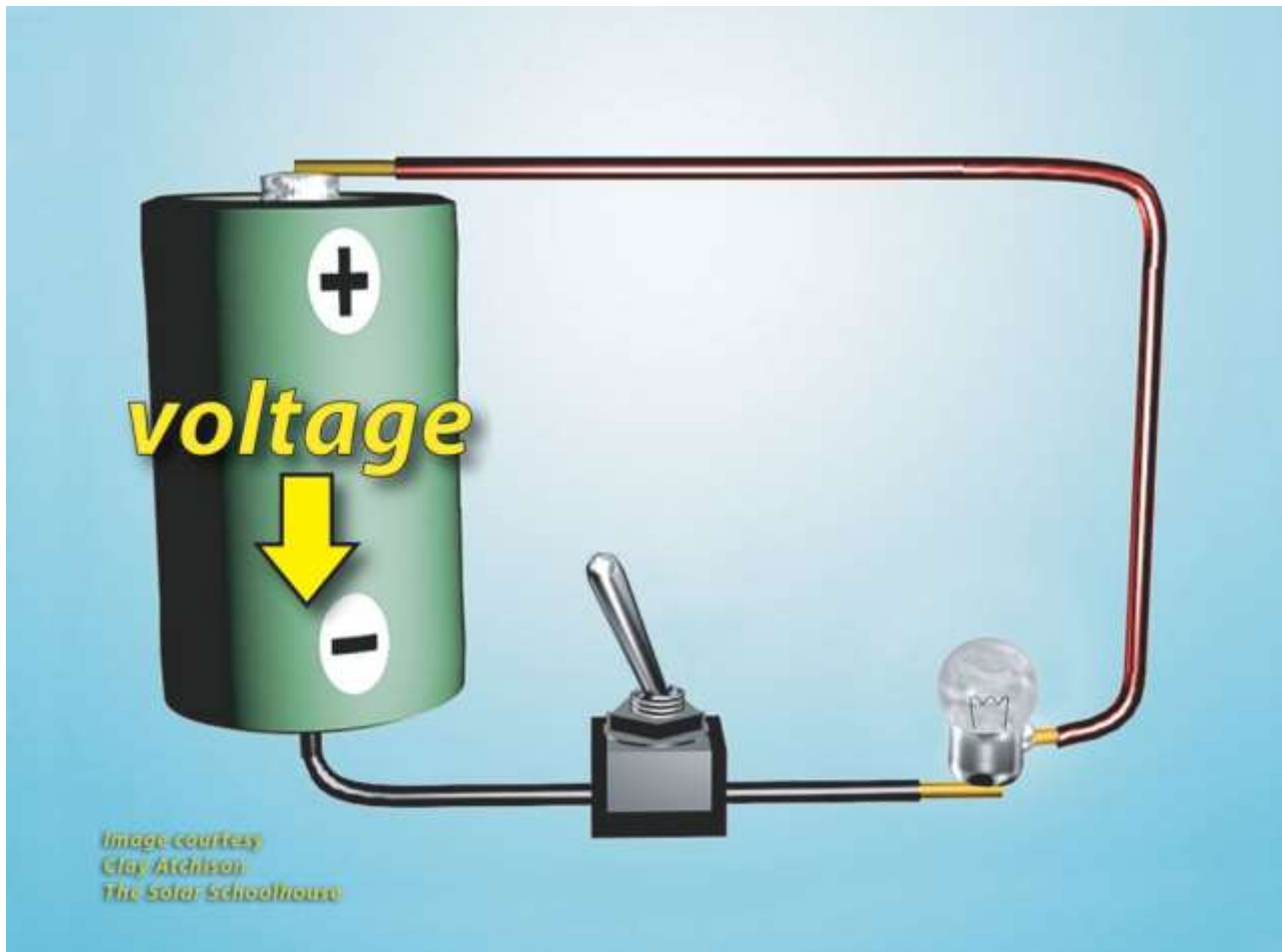Can we measure Amps?
Can we measure Volts?



Can we measure Amps now?

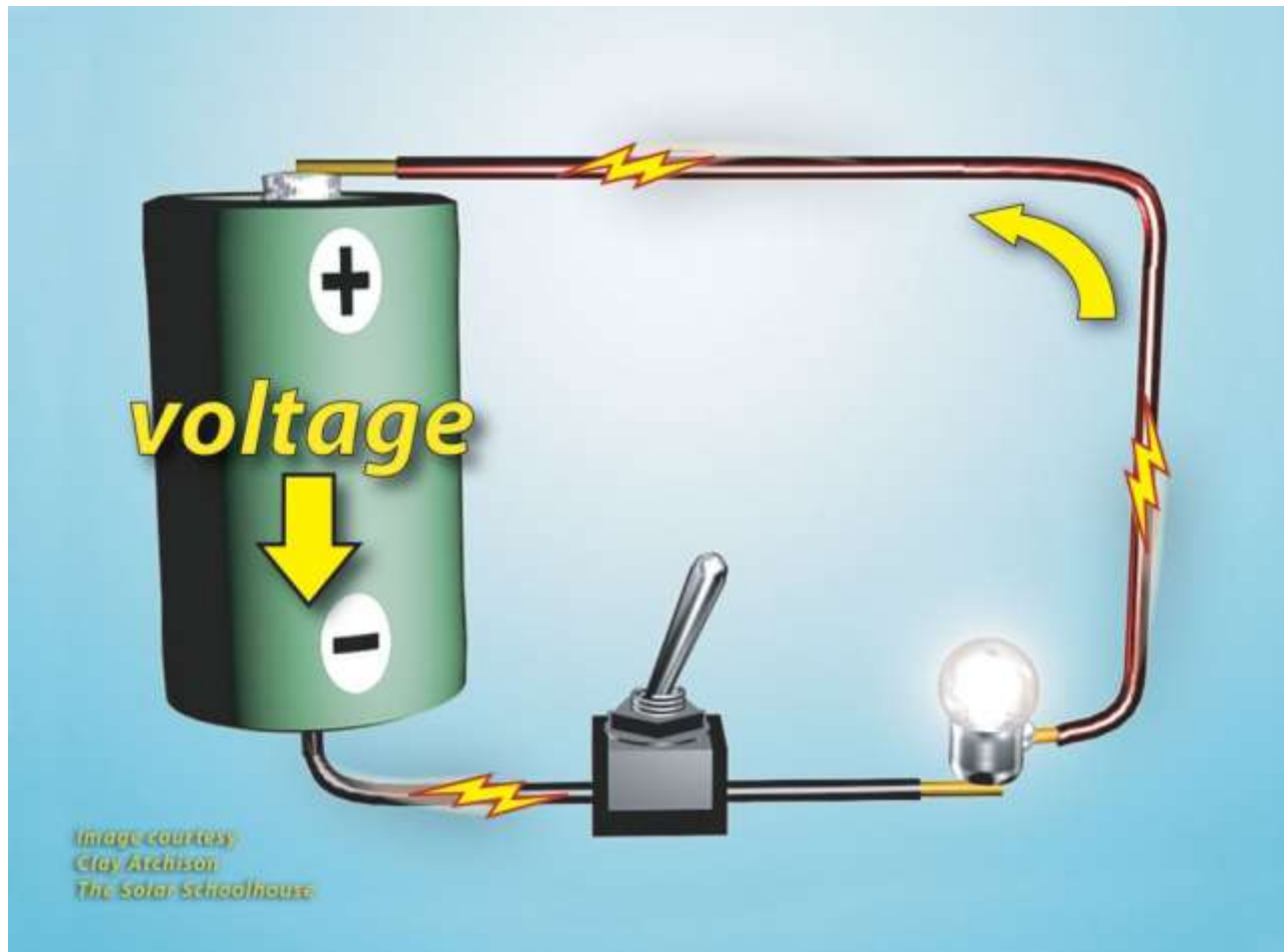How about Volts? How would you measure it?



Demonstration

Volts and Amps

Describe this River in terms of Volts and Amps



Compare this same Waterfall in two different seasons in terms of Volts and Amps





Watts is the Product of Volts and Amps

$$\text{Volts} \times \text{Amps} = \text{Watts}$$

$$12 \text{ volts} \times 5 \text{ amps} = 60 \text{ watts}$$

Watts is the Product of Volts and Amps

$$\text{Volts} \times \text{Amps} = \text{Watts}$$

Typical light bulb is 60 watts

$$120 \text{ volts} \times 0.5 \text{ amps} = 60 \text{ watts}$$

$$12 \text{ volts} \times 5 \text{ amps} = 60 \text{ watts}$$

PRACTICE

- Write Definitions for Volts, Amps, Watts.
Include the Water analogy
- Solve the Power Formula Equations on the
White board
- Share (and check) your answers with neighbor

Practice Using Power Formulas

- 2 volts x 2 amps = _____watts
- 4 volts x 2 amps = _____watts
- 12 volts x 2 amps = _____watts
- 12 volts x 10 amps = _____watts
- 24 volts x 20 amps = _____watts
- 500 volts x 10 amps = _____watts

The Photo Voltaic Effect: DeBrief

- First: Write in Journals:
- Second: Discussion
- Energy Transformation: Light → Electricity

Discuss their explorations: shade, orientation, reflection, concentration



Pressure of One Cylinder of Water



Double the height of the cylinder...




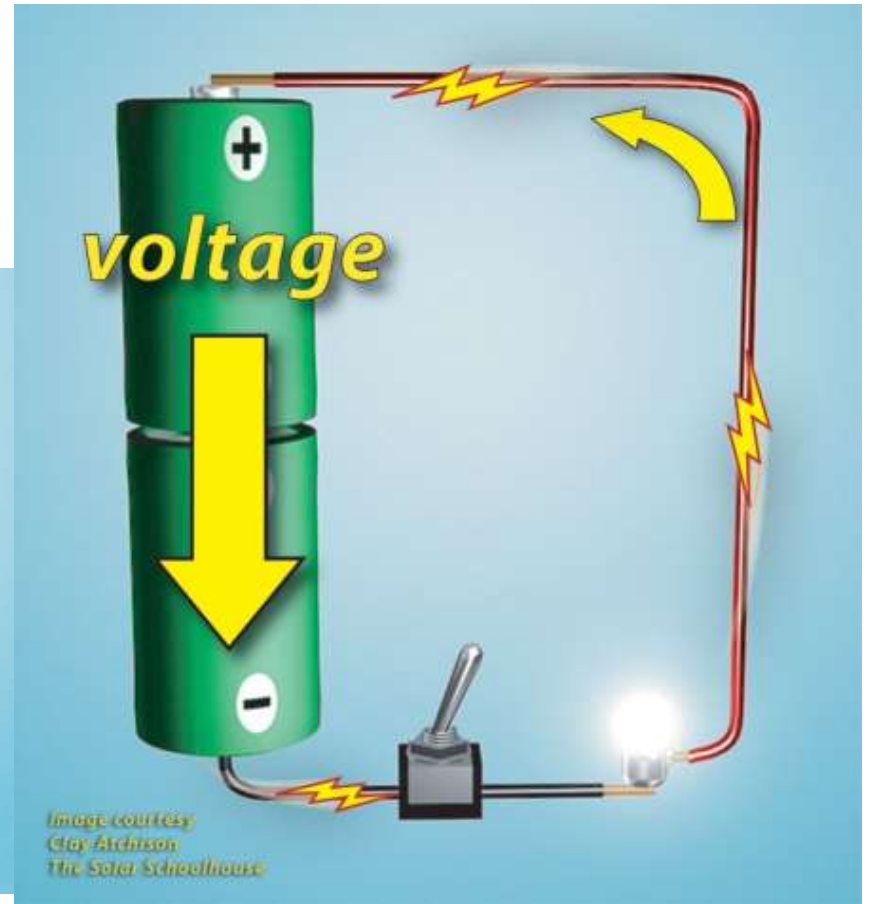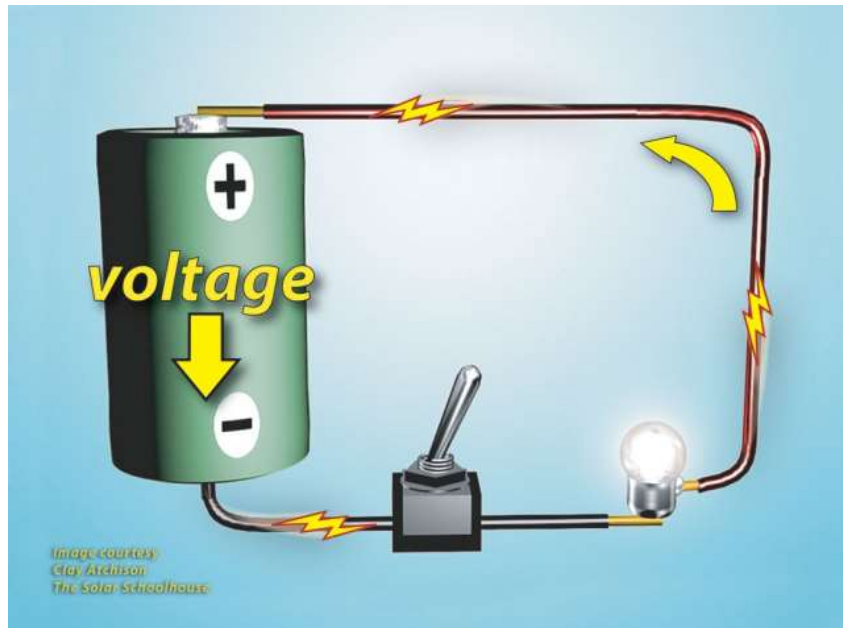In similar fashion when we double the battery in series (pos to neg)




In series wiring we wire the positive of one of the power sources to the negative terminal of the other power source. E.g. two batteries into a flashlight

1.5 volts
+
1.5 volts
= 3 volts

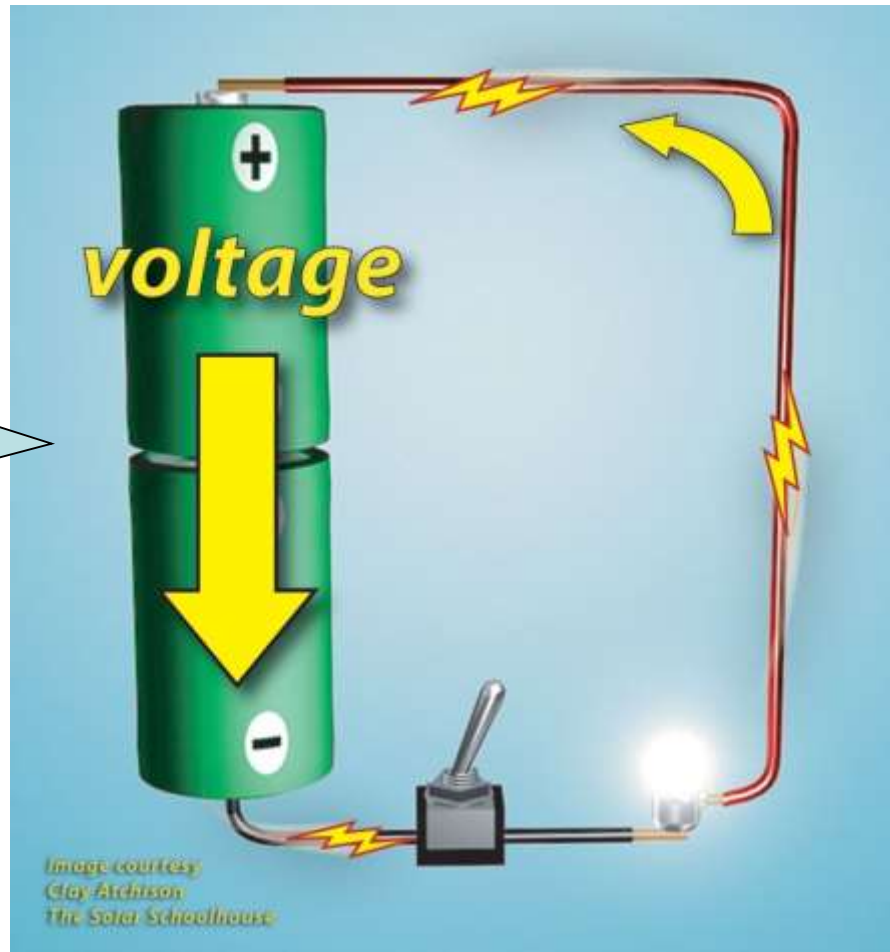


In series wiring Volts add up and amps stay constant

1.5 volts
+
1.5 volts
= 3 volts

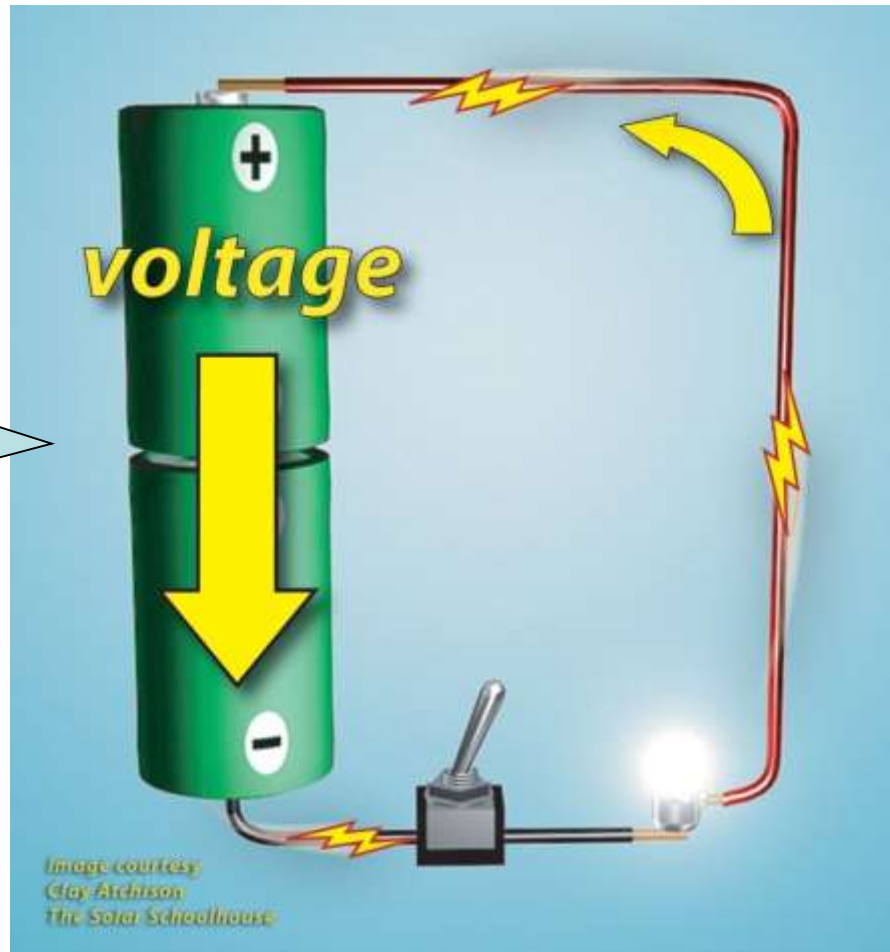


Copyright 2009 Hal Aronson

The same holds true for wiring Solar Modules in Series

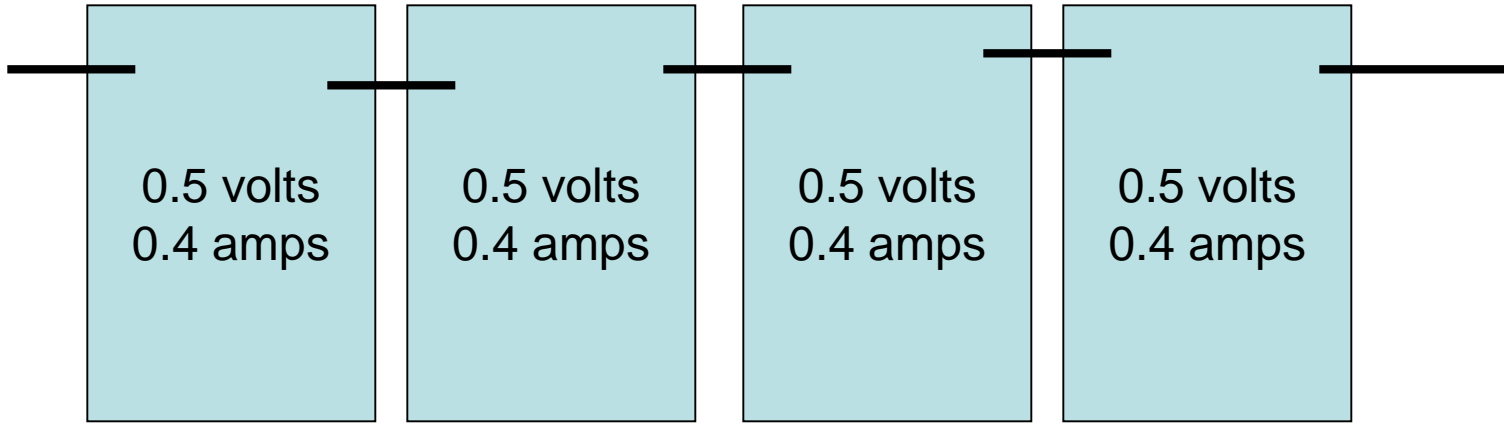

Four 0.5 volt modules in series will
produce
 $4 \times 0.5 \text{ volts} = 2 \text{ volts}$
The amperage will stay the same

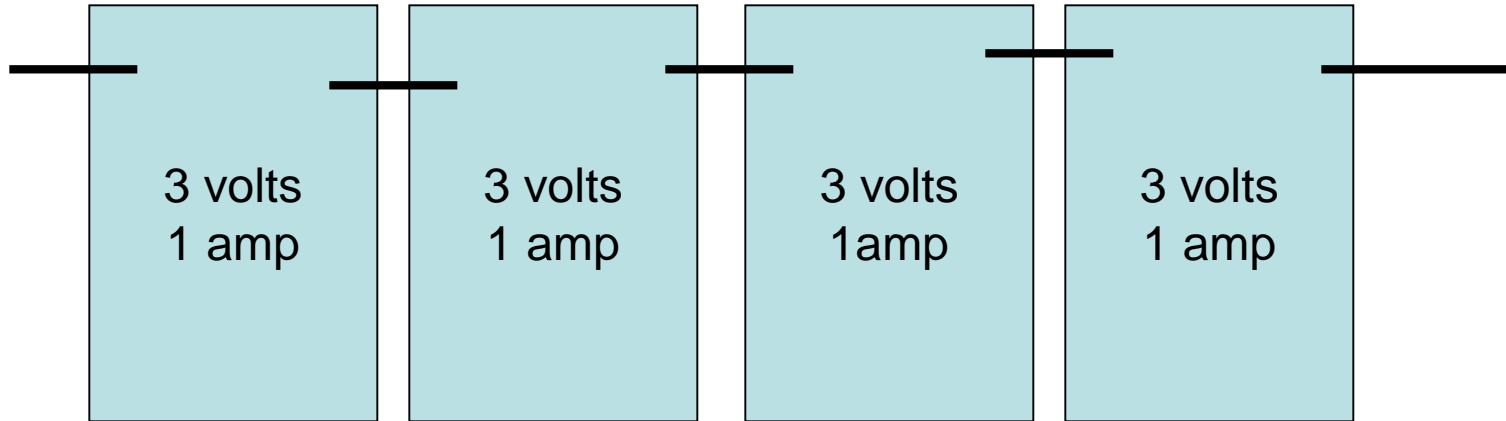The same holds true for wiring Solar Modules in Series



Parallel Wiring

- In parallel wiring, we connect the positive lead of one source to the positive lead of a second power source. In parallel wiring, the voltage stays the same, but the amps add up.

Wiring Solar Modules in Parallel and Parallel

